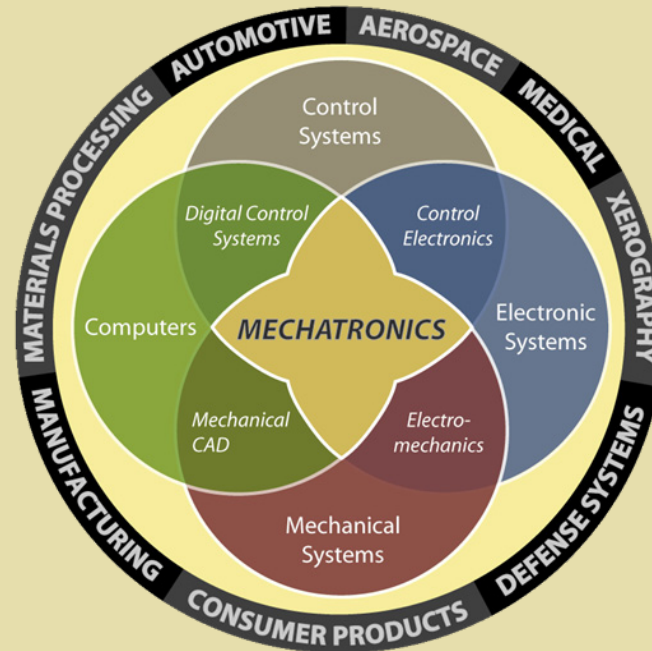


Electrical-Mechanical Analogy



Dr. Kevin Craig

Professor of Mechanical Engineering
Rensselaer Polytechnic Institute

Electrical – Mechanical Analogies

- A signal, element, or system which exhibits mathematical behavior identical to that of another, but physically different, signal, element, or system is called an analogous quantity or analog.

- Analogous quantities:

force \Leftrightarrow voltage

velocity \Leftrightarrow current

displacement \Leftrightarrow charge

damper \Leftrightarrow resistor


spring \Leftrightarrow capacitor

mass \Leftrightarrow inductor


- Force causes velocity, just as voltage causes current.
- A damper dissipates mechanical energy into heat, just as a resistor dissipates electrical energy into heat.
- Springs and masses store energy in two different ways (potential energy and kinetic energy), just as capacitors and inductors store energy in two different ways (electric field and magnetic field).

Spring Potential Energy	$\frac{1}{2} Kx^2 = \frac{1}{2} \frac{(Kx)^2}{K} = \frac{1}{2} \frac{f^2}{K}$	\Leftrightarrow	$\frac{1}{2} Ce^2 = \frac{1}{2} \frac{q^2}{C}$	Capacitor Electric Field Energy
Mass Kinetic Energy	$\frac{1}{2} Mv^2$	\Leftrightarrow	$\frac{1}{2} Li^2$	Inductor Magnetic Field Energy

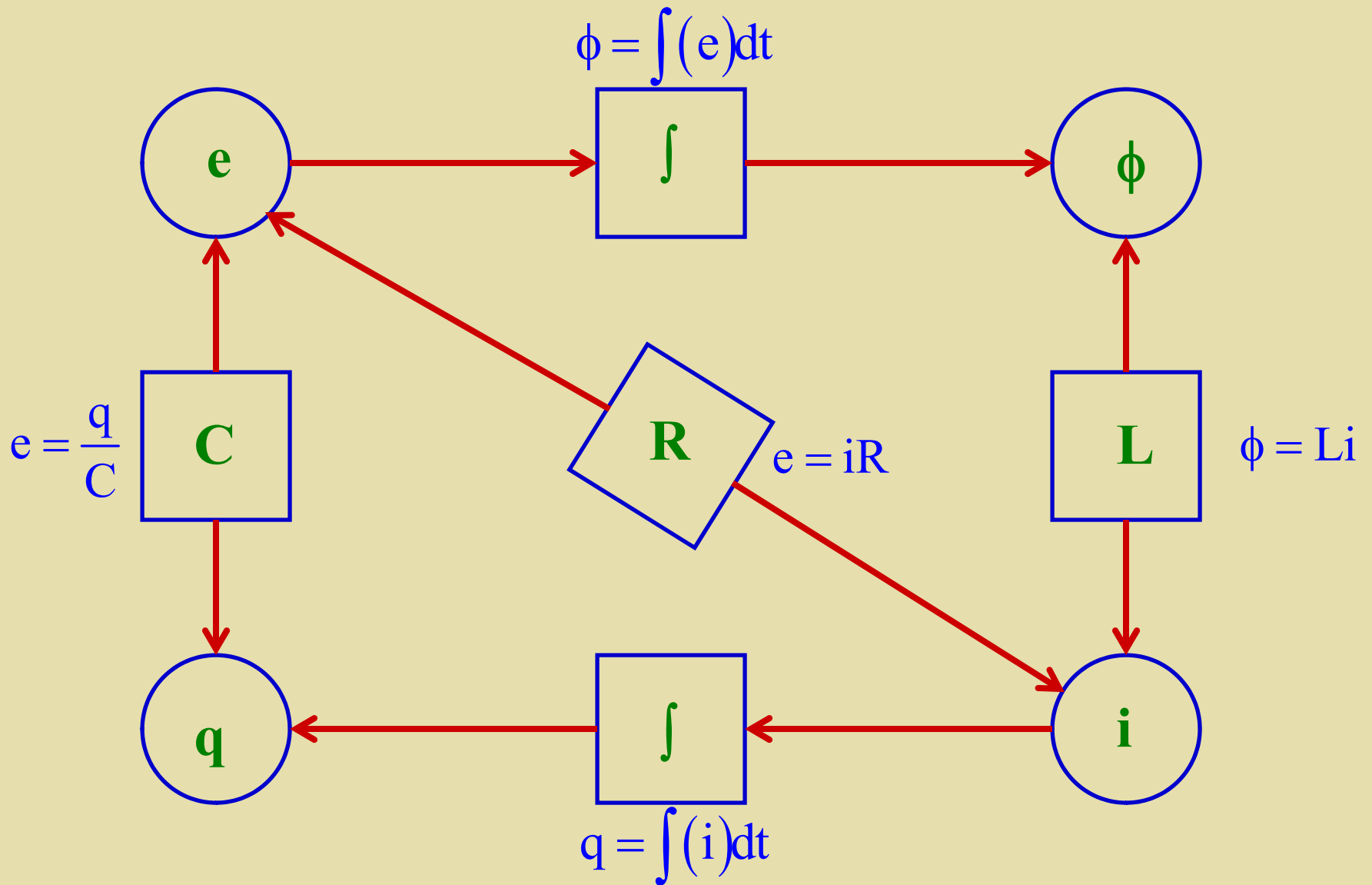- The product $(f)(v)$ represents instantaneous mechanical power, just as $(e)(i)$ represents instantaneous electrical power.



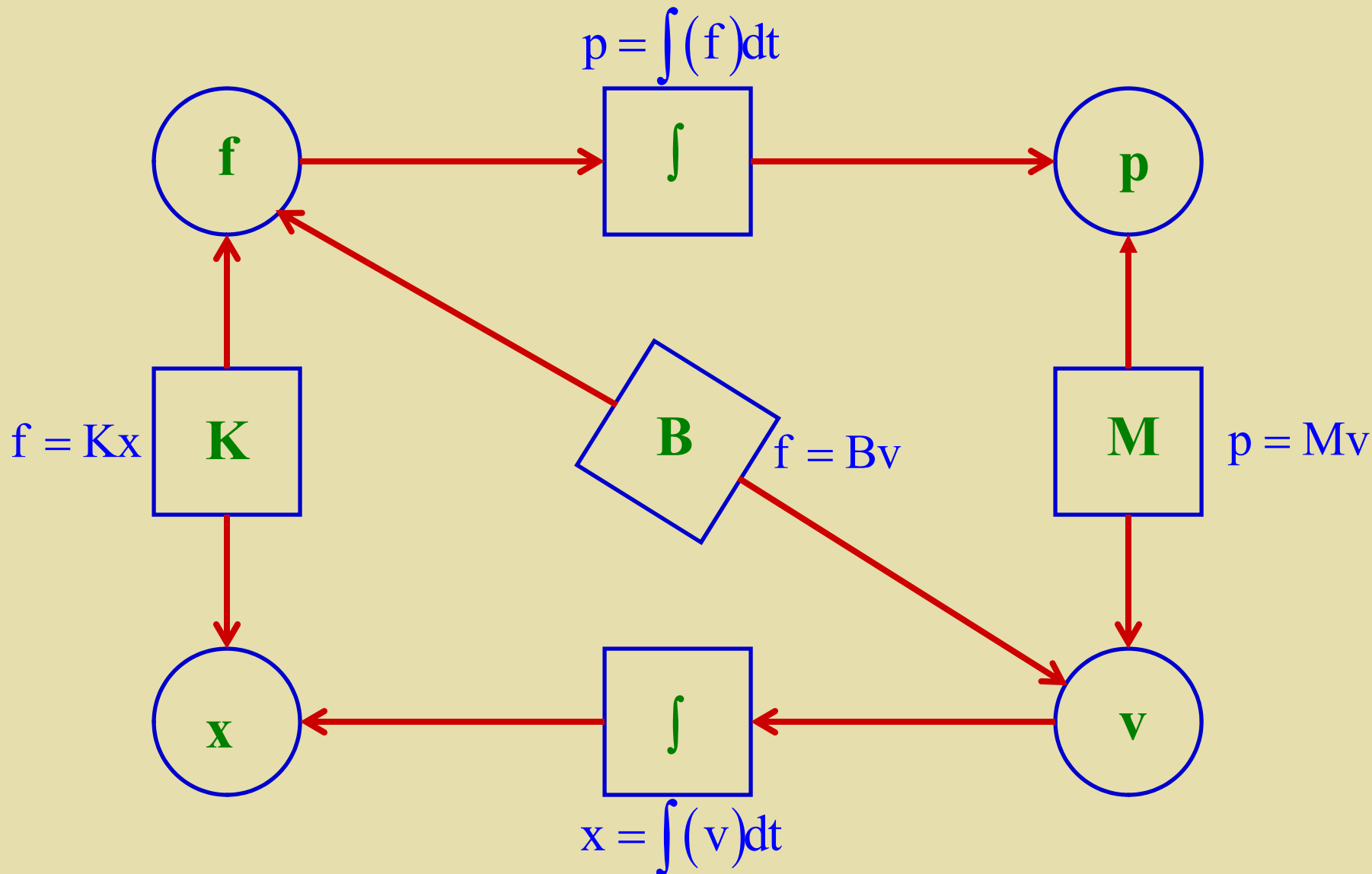General Model Structure for Electrical Systems



General Model Structure for Mechanical Systems

force $f \Leftrightarrow$ voltage e
 velocity $v \Leftrightarrow$ current i
 damper $B \Leftrightarrow$ resistor R
 spring $K \Leftrightarrow$ capacitor $1/C$
 mass $M \Leftrightarrow$ inductor L


Electrical – Mechanical Analogies

$$\text{Resistor } e = Ri \quad \Leftrightarrow \quad \text{Damper } f = Bv$$

$$\text{Inductor } e = L \frac{di}{dt} \quad \Leftrightarrow \quad \text{Mass } f = M \frac{dv}{dt}$$

$$\text{Capacitor } e = \frac{1}{C} \int i dt \quad \Leftrightarrow \quad \text{Spring } f = K \int v dt$$

RC Electrical System

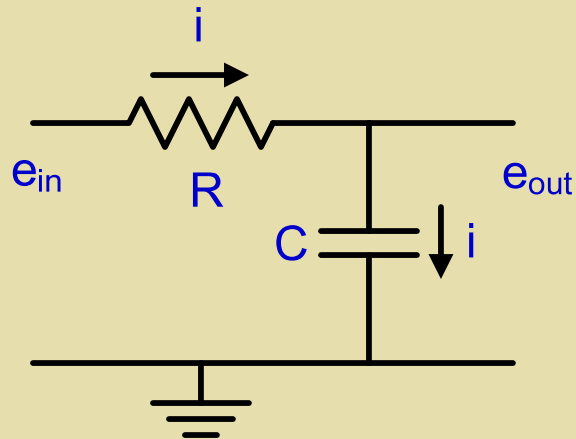

$$e_{in} - e_R - e_C = 0$$

$$e_{in} - iR - e_{out} = 0$$


$$e_{in} - \left(C \frac{de_{out}}{dt} \right) R - e_{out} = 0$$

$$RC \frac{de_{out}}{dt} + e_{out} = e_{in}$$

$$\frac{e_{out}}{e_{in}} = \frac{1}{RCD + 1} \quad \tau = RC$$

Electrical-Mechanical Analogy

Spring-Damper Mechanical System

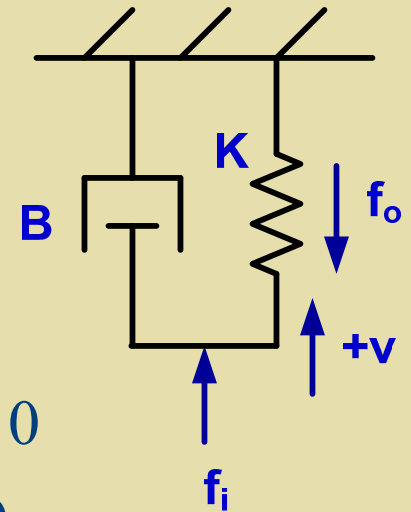

$$f_i - f_B - f_K = 0$$

$$f_i - Bv - KX = 0$$

$$f_i - Bv - f_o = 0$$


$$f_i - B \left(\frac{\dot{f}_o}{K} \right) - f_o = 0$$

$$\frac{B}{K} \dot{f}_o + f_o = f_i$$

$$\frac{f_o}{f_i} = \frac{1}{\frac{B}{K} D + 1} \quad \tau = \frac{B}{K}$$

K. Craig 7

LR Electrical System

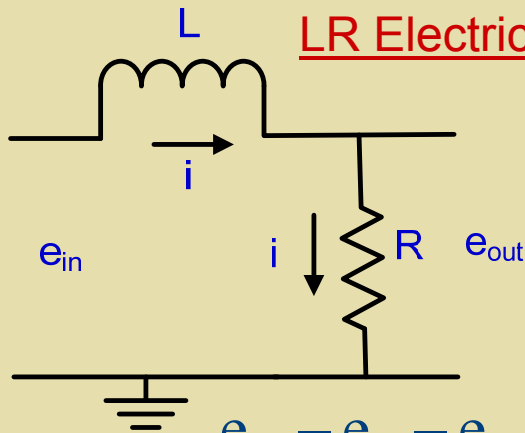

$$e_{in} - e_L - e_R = 0$$


$$e_{in} - L \frac{di}{dt} - e_{out} = 0$$

$$e_{in} - L \frac{d}{dt} \left(\frac{e_{out}}{R} \right) - e_{out} = 0$$

$$\frac{L}{R} \frac{de_{out}}{dt} + e_{out} = e_{in}$$

$$\frac{e_{out}}{e_{in}} = \frac{1}{\frac{L}{R} D + 1} \quad \tau = \frac{L}{R}$$

Mass-Damper Mechanical System

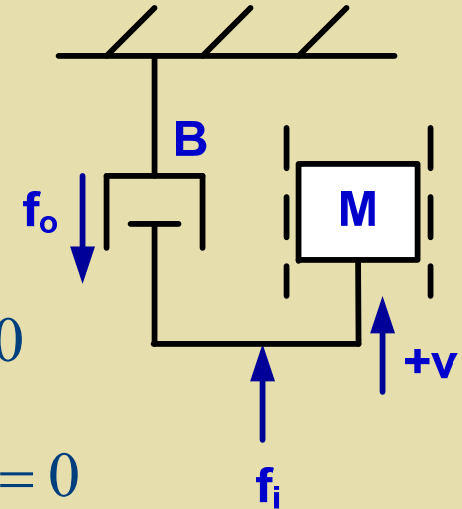

$$f_i - f_B - f_M = 0$$


$$f_i - Bv - M \dot{v} = 0$$

$$f_i - f_o - M \left(\frac{\dot{f}_o}{B} \right) = 0$$

$$\frac{M}{B} \dot{f}_o + f_o = f_i$$

$$\frac{f_o}{f_i} = \frac{1}{\frac{M}{B} D + 1} \quad \tau = \frac{M}{B}$$

LRC Electrical System

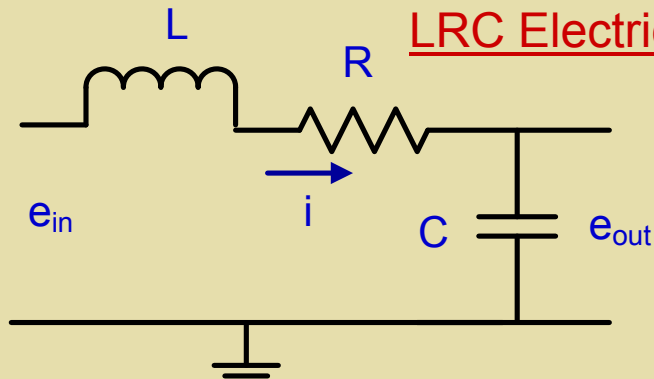

$$e_{in} - e_L - e_R - e_C = 0$$

$$e_{in} - L \frac{di}{dt} - Ri - e_{out} = 0$$


$$e_{in} - L \frac{d}{dt} \left(C \frac{de_{out}}{dt} \right) - R \left(C \frac{de_{out}}{dt} \right) - e_{out} = 0$$

$$LC \frac{d^2 e_{out}}{dt^2} + RC \frac{de_{out}}{dt} + e_{out} = e_{in}$$

$$\frac{e_{out}}{e_{in}} = \frac{1}{LCD^2 + RCD + 1} = \frac{K_S}{\frac{1}{\omega_n^2} D^2 + \frac{2\zeta}{\omega_n} D + 1}$$

$$\omega_n = \sqrt{\frac{1}{LC}} \quad \zeta = \frac{R}{2} \sqrt{\frac{C}{L}} \quad K_S = 1$$

Mass-Spring-Damper Mechanical System

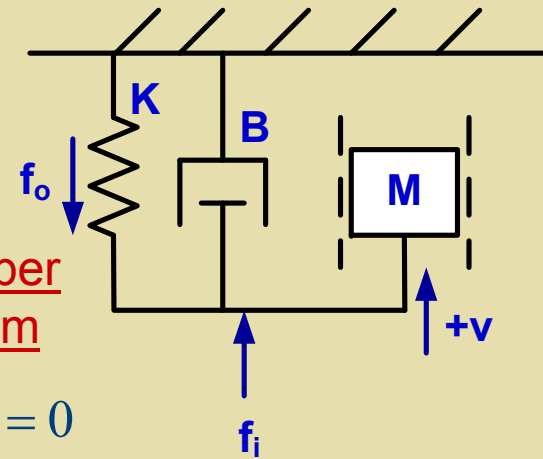

$$f_i - f_K - f_B - f_M = 0$$

$$f_i - Kx - Bv - M\dot{v} = 0$$


$$f_i - f_o - B \left(\frac{\dot{f}_o}{K} \right) - M \left(\frac{\ddot{f}_o}{K} \right) = 0$$



$$\frac{M}{K} \ddot{f}_o + \frac{B}{K} \dot{f}_o + f_o = f_i$$




$$\frac{f_o}{f_i} = \frac{1}{\frac{M}{K} D^2 + \frac{B}{K} D + 1} = \frac{K_S}{\frac{1}{\omega_n^2} D^2 + \frac{2\zeta}{\omega_n} D + 1}$$

$$\omega_n = \sqrt{\frac{K}{M}} \quad \zeta = \frac{B}{2} \sqrt{\frac{1}{KM}} \quad K_S = 1$$

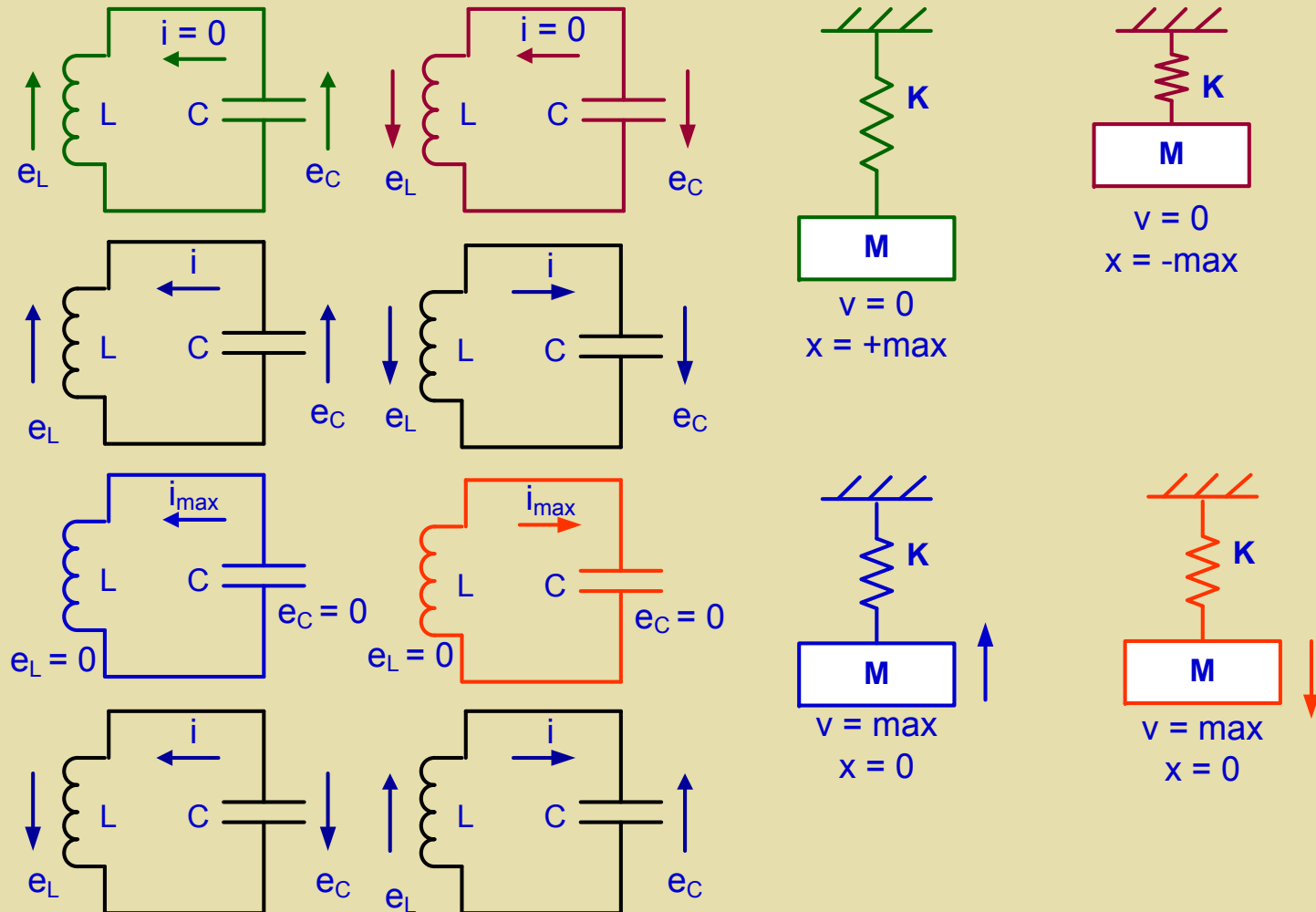- Inductor-Capacitor (LC) ↔ Mass-Spring (MK)
Oscillations



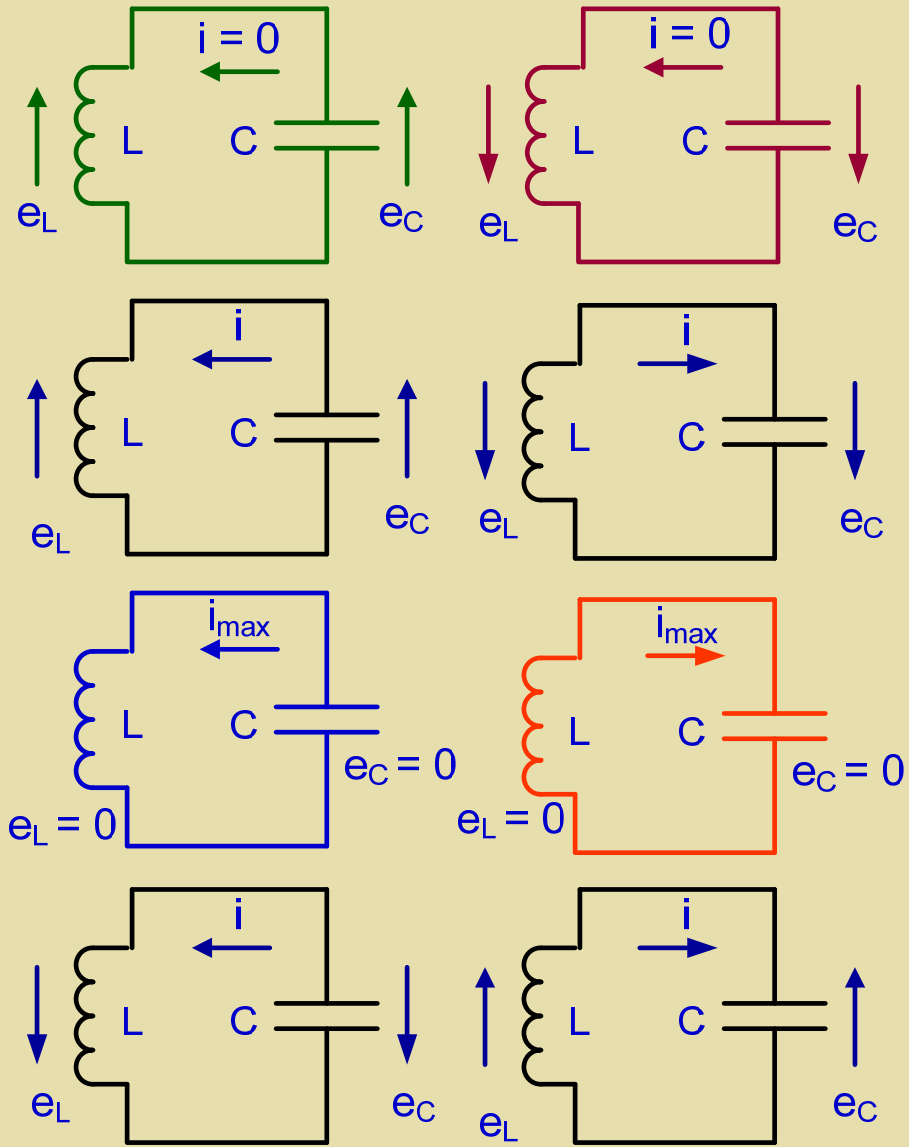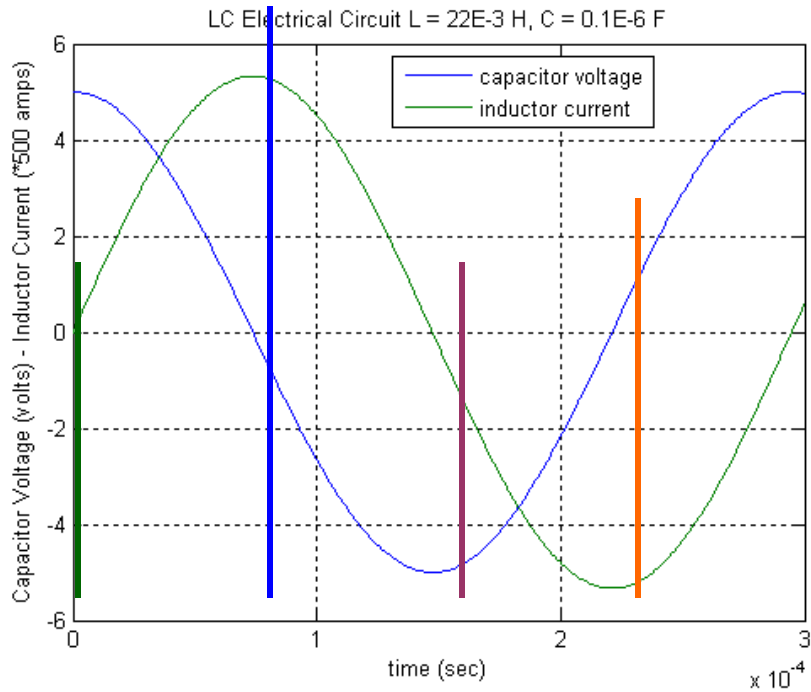

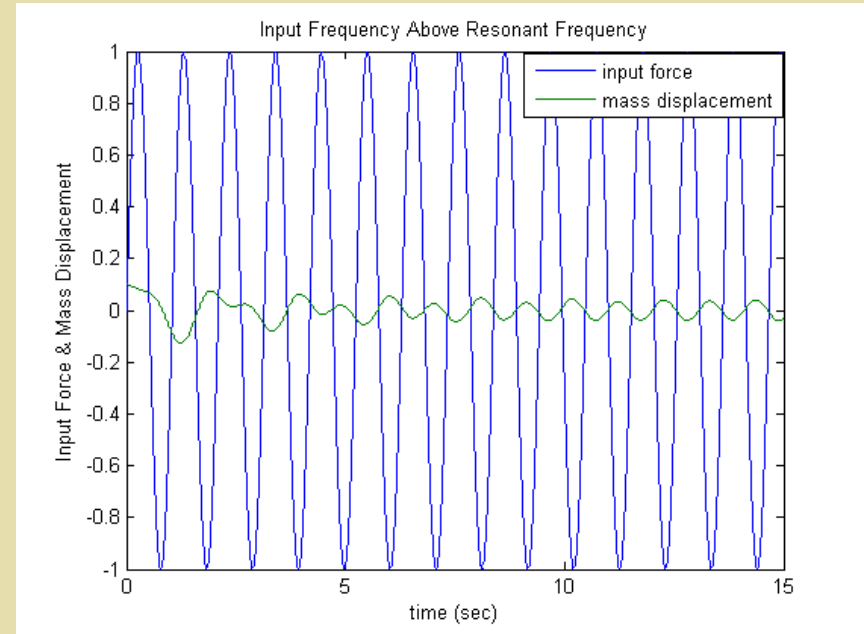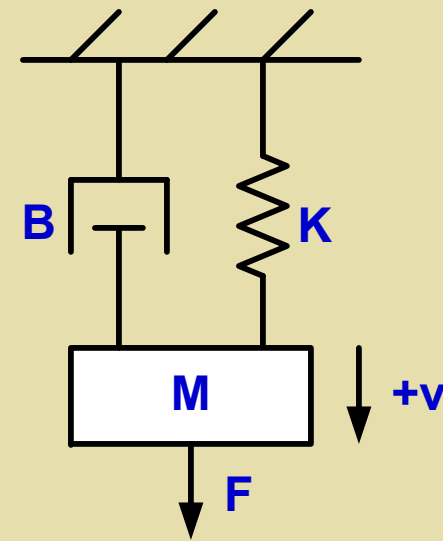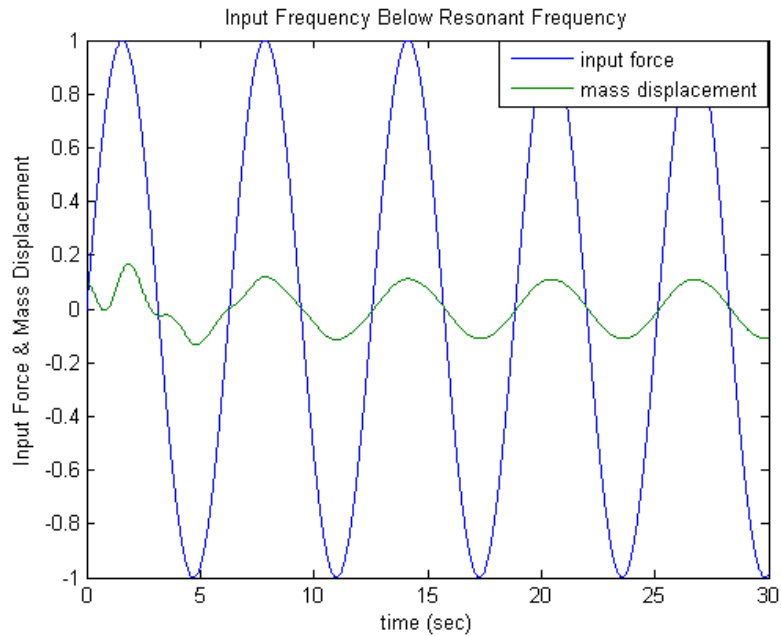

Resonance

